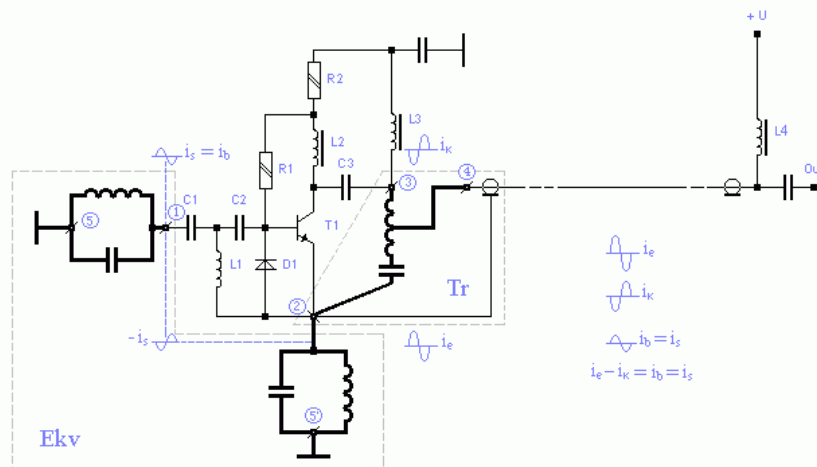


Pic. 3. Active Antenna (Aerial) Circuit with Minus Power Supply.

On pic. 2 and pic. 3 nonselective one-stage amplifier (transistors KT3101, KT372) is mounted directly in a dipole.



Pic. 4. Amplifier Circuit and Dipole Equivalent Circuit (with Plus Power Supply).